

## Unit V → Logic gates -

- ① AND ✓
- ② OR ✓
- ③ NOT (Inverter) ✓

## Binary number system

→ Base-2 (~~B-2~~ Binary)

0.  
1.

## Boolean functions -

$$\begin{array}{c} 0, 1 \\ \hline A + A = A \end{array}$$

$$\begin{array}{c} 0, 1 \\ \hline A \cdot A = A \end{array}$$

$$\begin{array}{c} 0, 1 \\ \hline A \cdot \bar{A} = 0 \end{array}$$

$$\begin{array}{c} 1 \\ \hline \bar{\bar{A}} = A \end{array}$$

$$1 + A = 1$$

$$A = \underline{0, 1}$$

## Boolean Algebra .

Decimal (B-10)

0  
⋮  
9

$$\bar{0} + \bar{0} = 0$$

$$0 + \bar{1} = 1$$


$$1 + 0 = 1$$

$$1 \cdot 0 = 0$$

$$1 \cdot \bar{1} = 1$$

$$1 + 1 = 1$$

# ① NOT Gate - (Inverter)

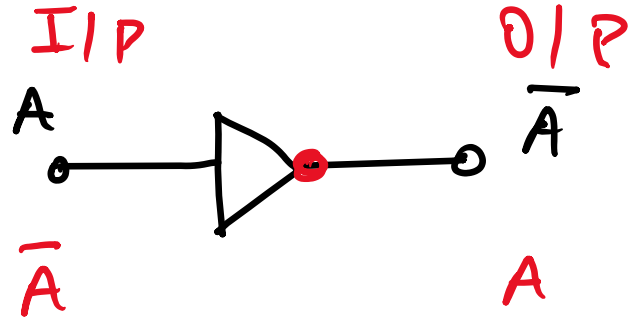


## Truth table -

I/P	O/P
A	$\bar{A}$
0	1
1	0

) → Inverted o/p


# ② AND Gate

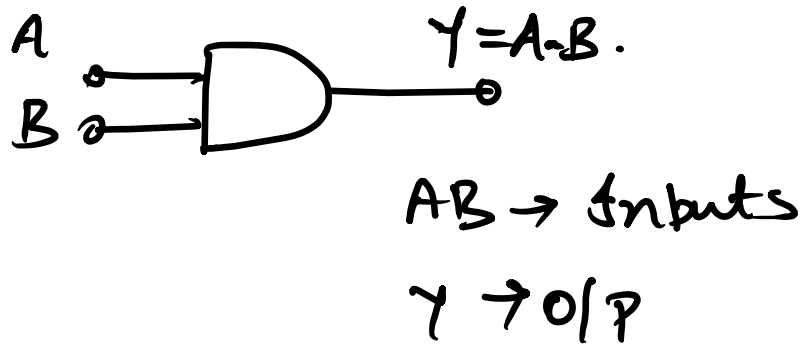


## Truth table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


## Circuit

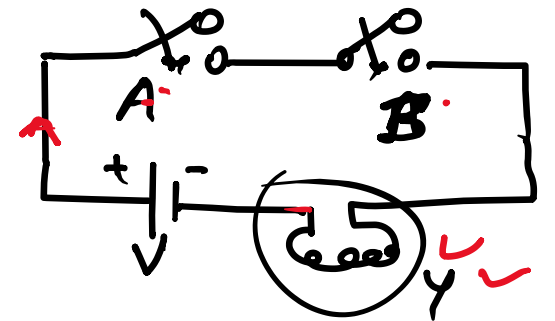

### ③ OR-Gate-

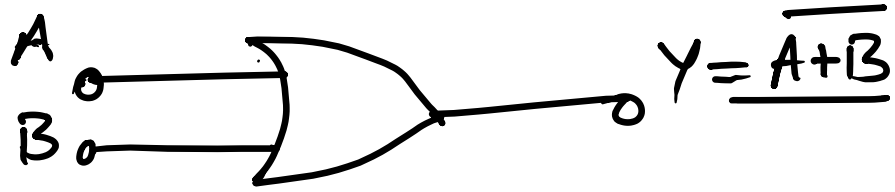



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

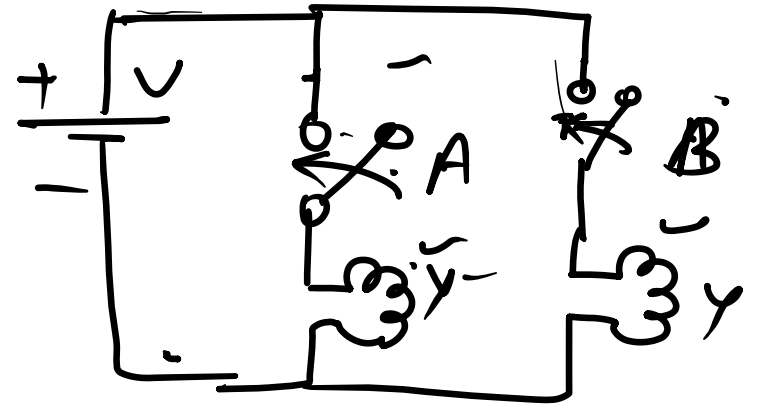

### → Universal Gates.


① NAND → AND + NOT

② NOR → OR + NOT

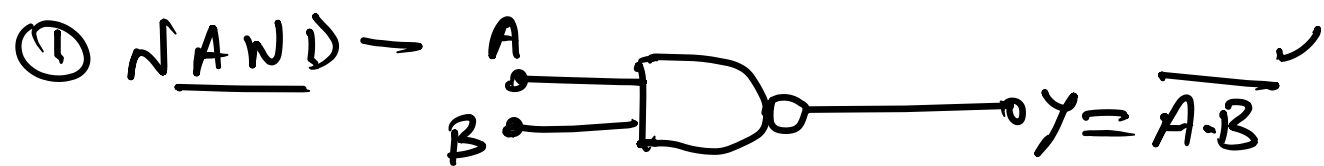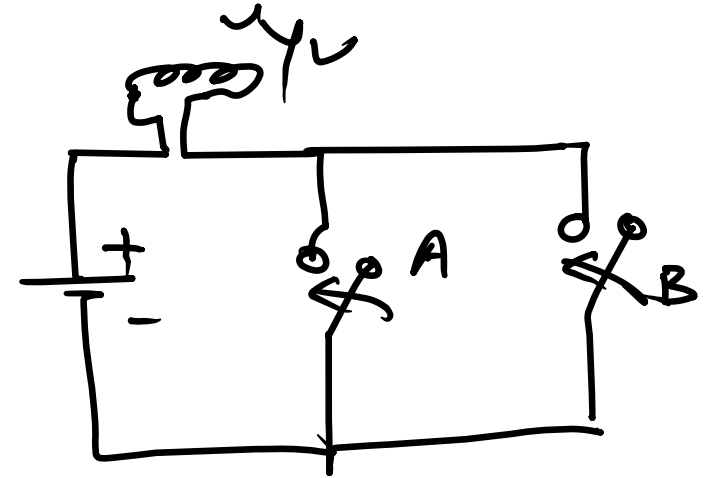

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

## ② NOR Gate -

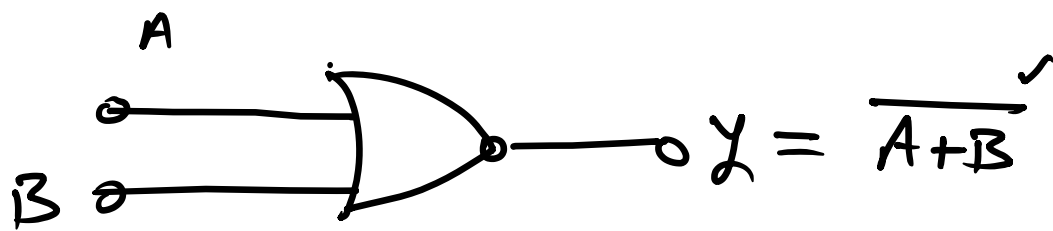

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

The operation of every gate can be performed using

NOR & NAND Gate, so these are called as universal Gates.